

Date:22-08-2025

LAB-2



Group Members:

Nandakishor P B-2023BEC0031

Sandeep varma -2023BEC0032


Vaishnavi -2023BEC0030

INVERTER:

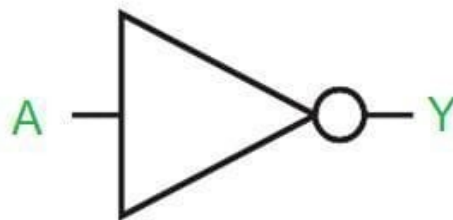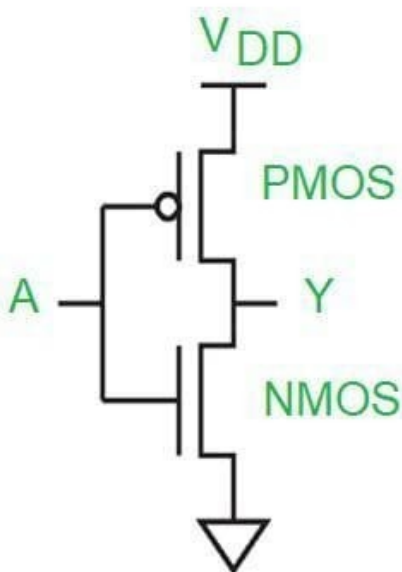


A	Y
0	1
1	0


SCHEMATIC DIAGRAM:

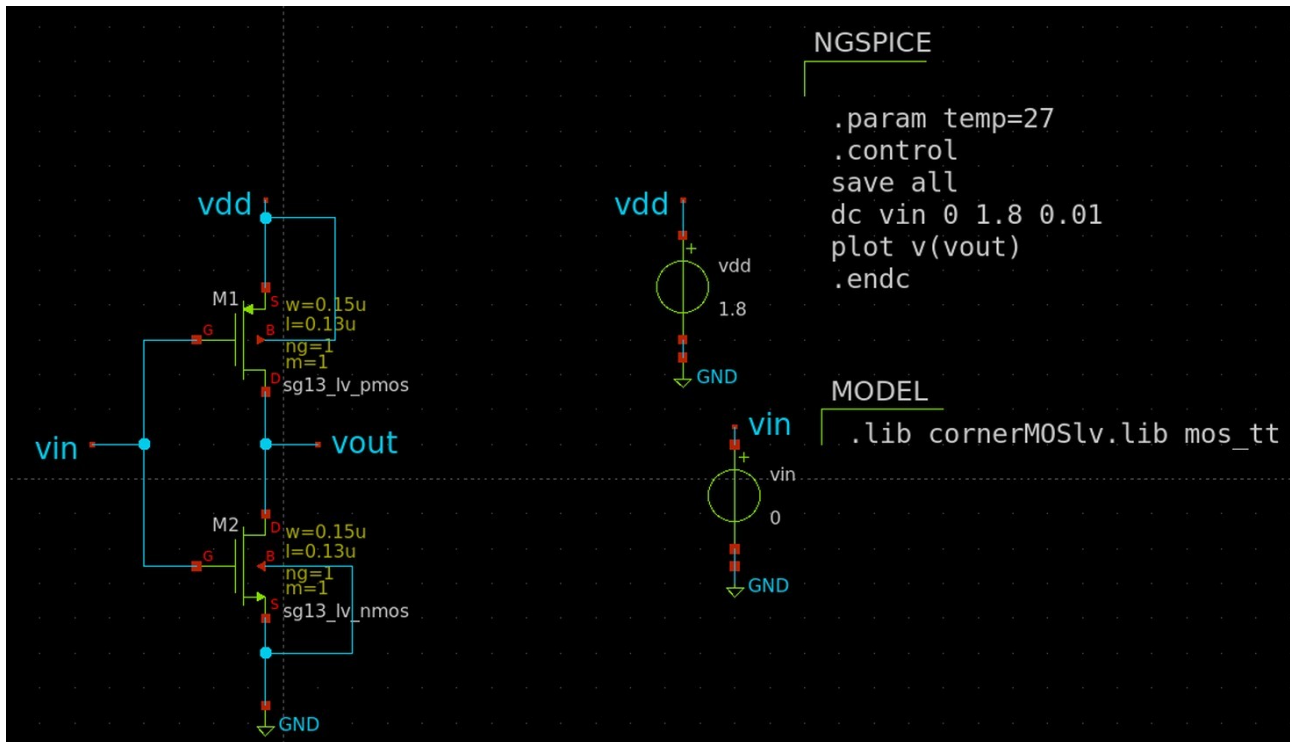

DC ANALYSIS:

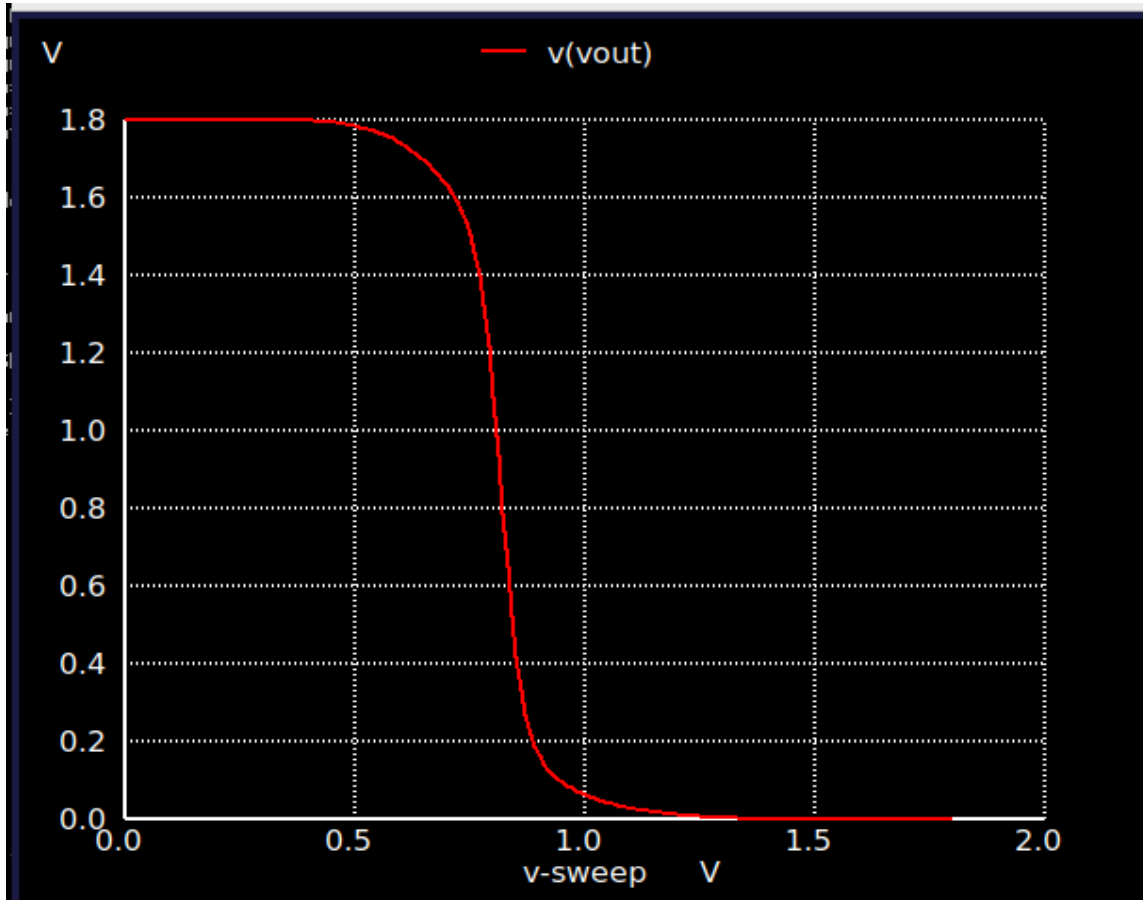

AC ANALYSIS:

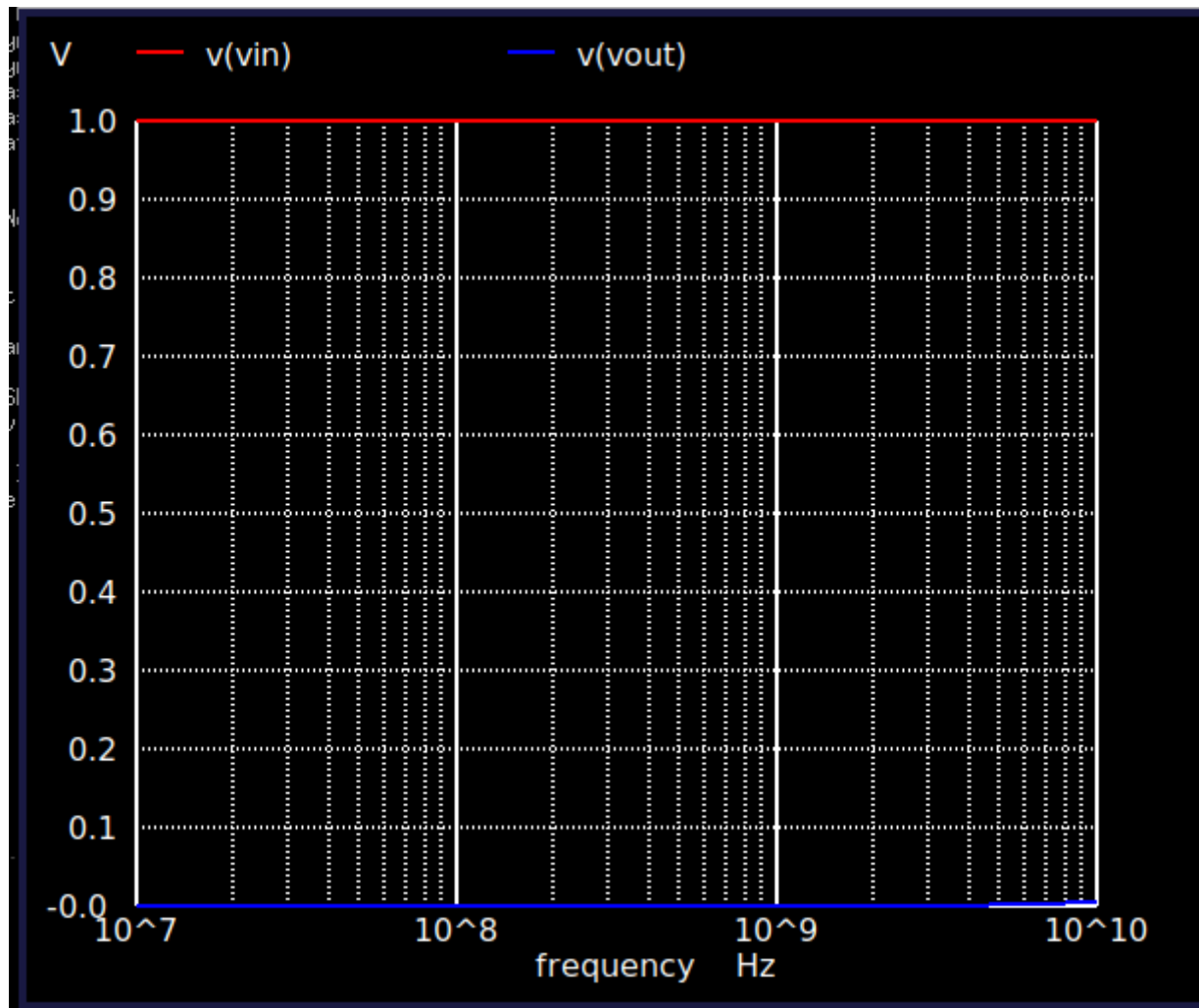

Inference:

*Successfully completed inverter experiment.

*we have given input values 0v to 1.8v and observed dc characteristics of the waveform.

Tools used:

XSCHEM(schematic editor)

Ngspice-44.2(spice simulations)

Library used IHP-130nm Pdk